

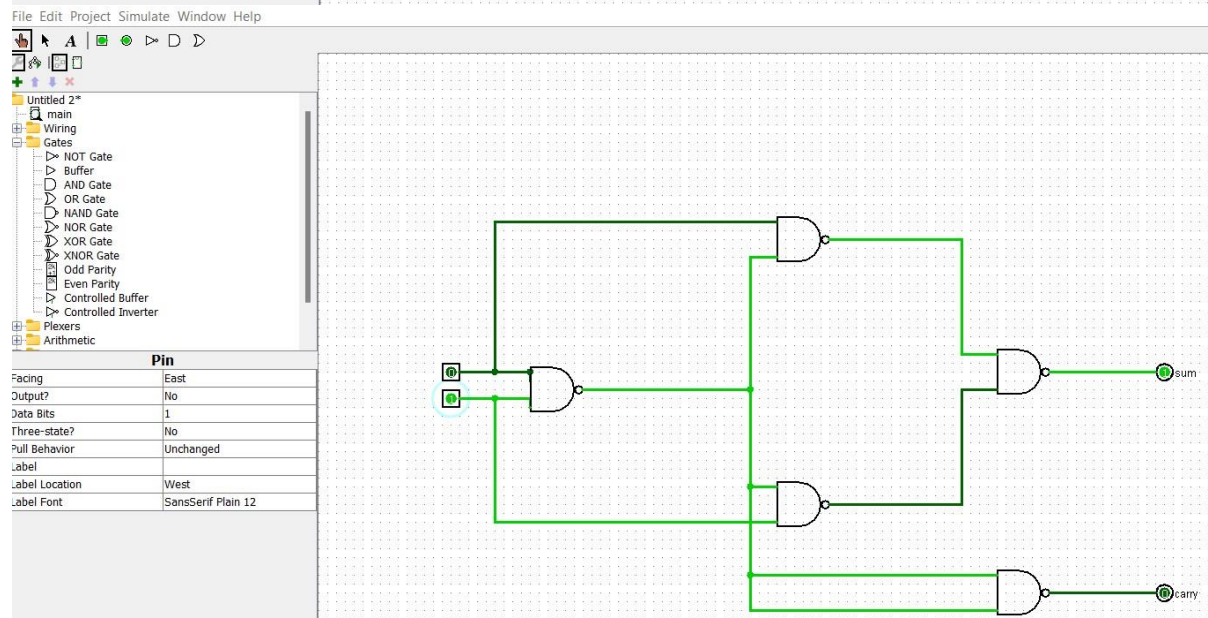



## 11) 2 BIT HALF ADDER USING NAND GATES

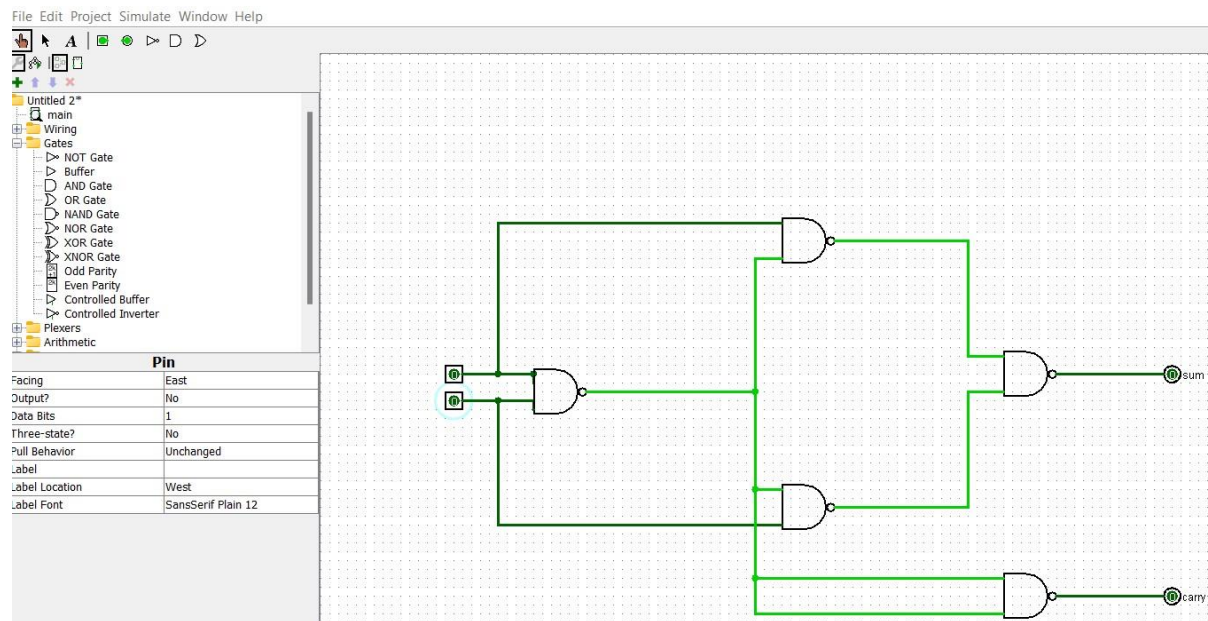


File Edit Project Simulate Window Help

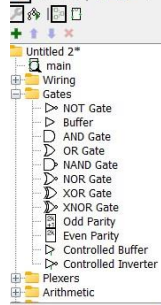

Pin	
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

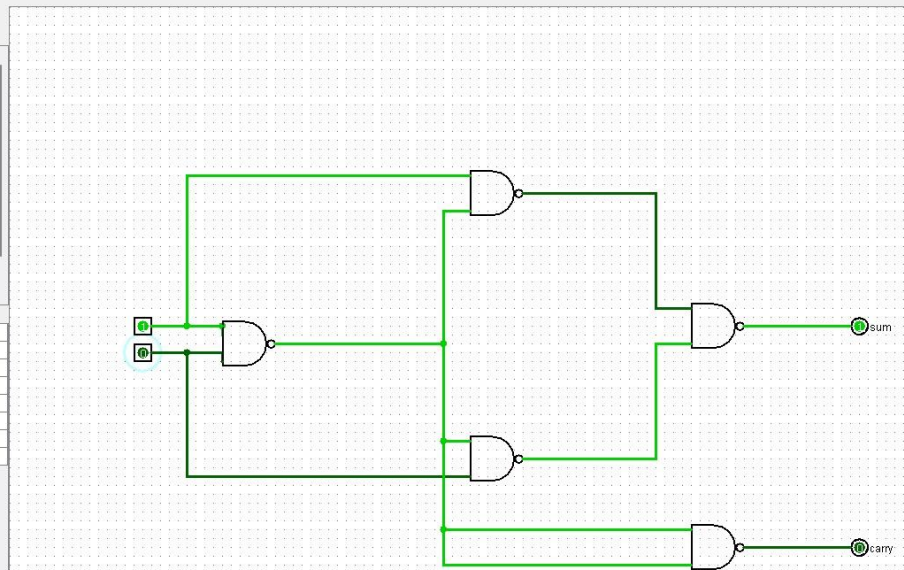

File Edit Project Simulate Window Help

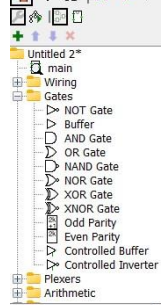

Pin	
Facing	East
Output?	No
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	
Label Location	West
Label Font	SansSerif Plain 12

